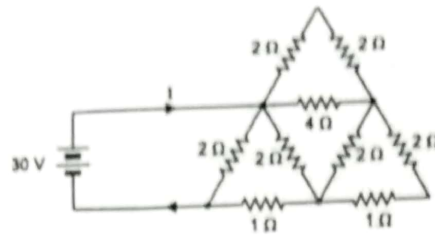


1. Find the power supplied by the voltage source

$$R_{eq} = 1.055 \Omega$$


$$I = 28.45 A$$

$$P = 853.6 W$$



2. Determine current in  $4\Omega$  resistance using Kirchhoff's laws

$$I_{4\Omega} = 4.1 A$$

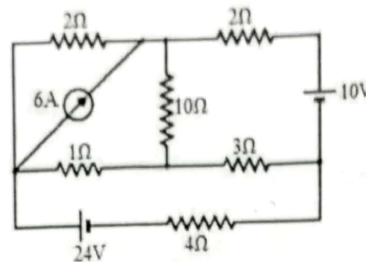


3. In the circuit shown in figure, calculate  $I$ ,  $I_1$  and  $V_{ab}$ .

$$I = 4 A$$

$$I_1 = 0.25 A$$

$$V_{AB} = 4 V$$


$$R_{eq} = 6 \Omega$$

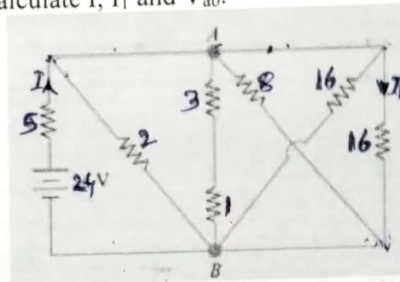

4. If the total power dissipated in the circuit is 16 W, calculate the value of ' $R$ ' & the total current.

$$R = 6 \Omega$$

$$I = 2 A$$

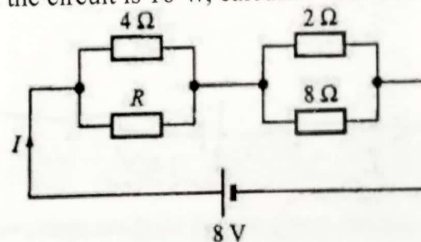

5. Determine the voltage across and current through each resistor in the circuit.


$$V_1 = V_2 = 30 V$$

$$V_3 = 50 V$$

$$I_1 = 7.5 A$$

$$I_2 = 2.5 A$$

$$I = 10 A$$

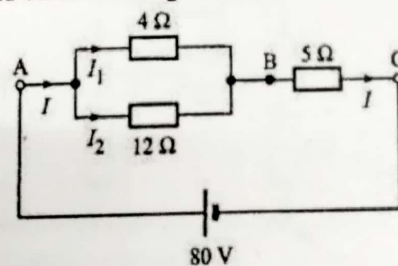


6. Using nodal analysis find the current in different resistances

$$V_A = -1.5 V$$

$$V_B = 0.7 V$$

$$V_C = -1.6 V$$

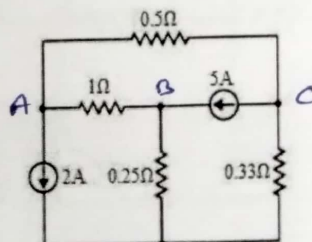


7. Find the current  $I$  using nodal analysis. All resistances are given in  $\Omega$

$$V_A = 1.5 \text{ V}$$

$$V_B = 1.75 \text{ V}$$

$$V_C = 3.75 \text{ V}$$

$$I = 2 \text{ A}$$

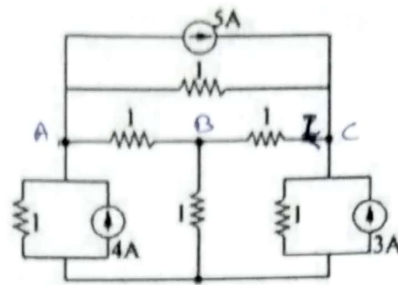


8. Using nodal analysis find the power supplied by 14V battery

$$V_A = 7 \text{ V}$$

$$V_B = 7 \text{ V}$$

$$I_{14V} = \frac{7}{4} \text{ A}$$

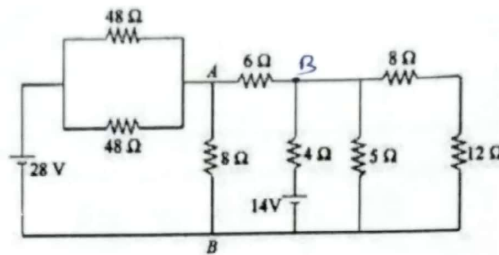


9. Find the voltage  $v$  using Nodal analysis

$$v = 19 \text{ V}$$

$$V_A = 19 \text{ V}$$

$$V_B = 42.6 \text{ V}$$

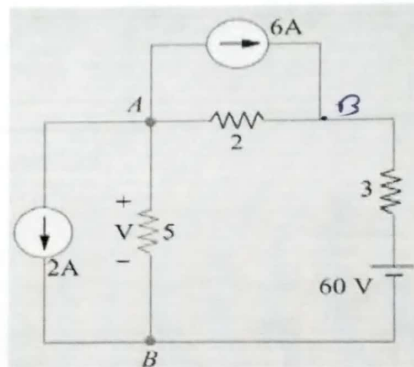


10. Find the current ' $I$ ' using node-voltage analysis for the given circuit.

$$V_1 = 3.82 \text{ V}$$

$$V_2 = 2.36 \text{ V}$$

$$I = -2.27 \text{ A}$$

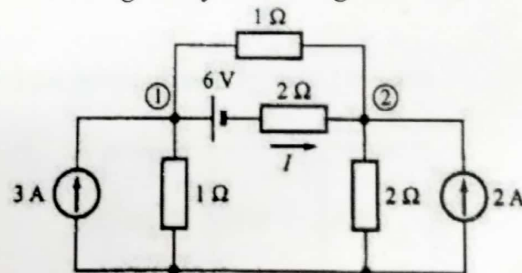


11. Evaluate current in  $4\Omega$  resistance using nodal analysis

$$V_A = 9.2 \text{ V}$$

$$V_B = 11.2 \text{ V}$$


$$I = 0.75 \text{ A}$$

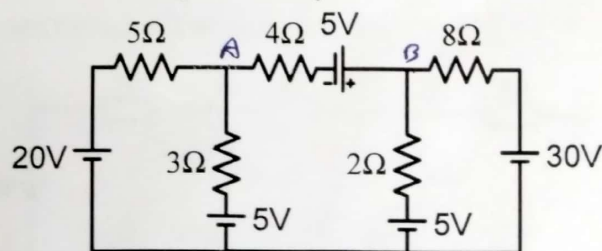

12. Using nodal analysis find the current in  $5\ \Omega$  resistance.


$$I = 0.307\text{ A}$$

$$V_A = 1.535\text{ V}$$

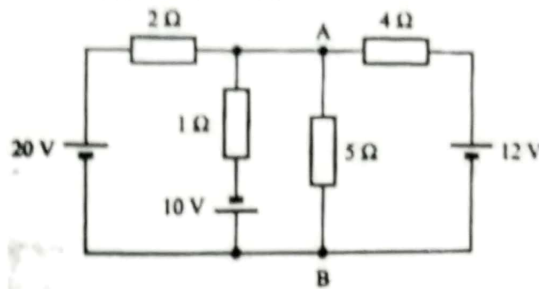

13. Using nodal analysis find the current in  $3\ \Omega$  resistance.

$$I = 0.5\text{ A}$$

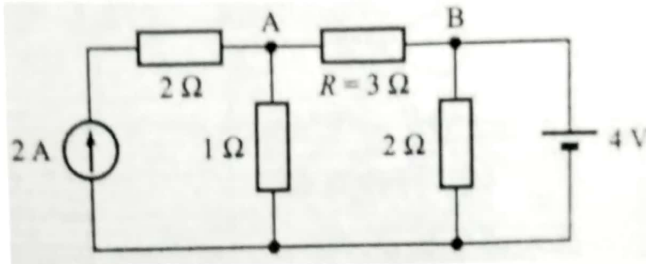


14. Using nodal voltage method calculate the magnitude and direction of current through  $10\ \Omega$  resistor.

$$V_1 = 10.07\text{ V}$$

$$V_2 = 30.59\text{ V}$$

$$I = 2.05\text{ A}$$

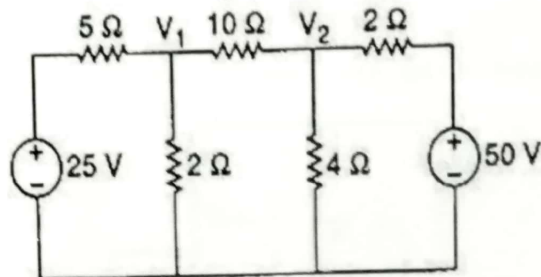


15. Using nodal analysis find the current  $i_x$ .

$$V_1 = 25.89\text{ V}$$

$$V_2 = 20.31\text{ V}$$

$$V_3 = -19.89\text{ V}$$

$$I_x = 2.79\text{ A}$$

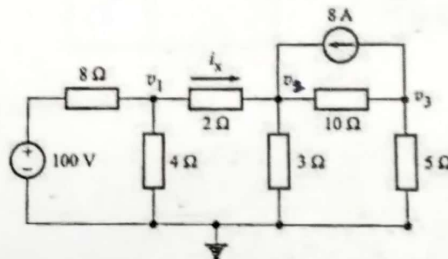


16. Using nodal analysis, find the power dissipated in  $2\ \Omega$  resistor.

$$V_A = 60\text{ V}$$

$$V_B = 6\text{ V}$$

$$I = 2\text{ A}$$

$$P = 8\text{ W}$$

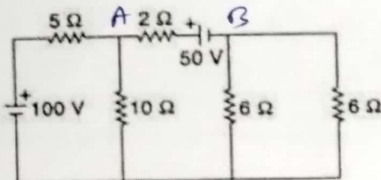


17. Find the value of current through  $5\ \Omega$  using node voltage method.

$$V_A = 27\text{ V}$$

$$V_B = 10\text{ V}$$


$$I_{5\Omega} = 8\text{ A}$$

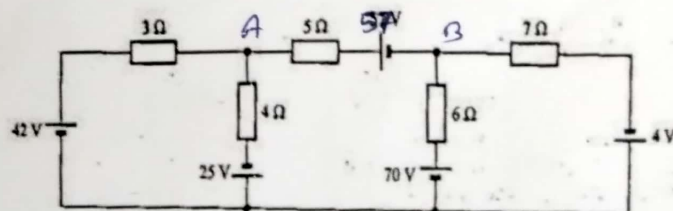

18. Using mesh analysis find the current in  $4\Omega$  and  $20\Omega$  resistance

$$I_{4\Omega} = 0.75 \text{ A}$$

$$I_{20\Omega} = 0.375 \text{ A}$$

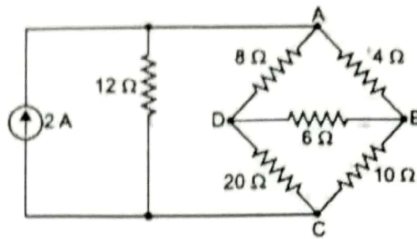


19. Find the value of  $E$  such that the current in  $4\Omega$  resistance is  $0\text{A}$ . Use mesh analysis method

$$E = 12 \text{ V}$$

$$I_1 = 2.13 \text{ A}$$

$$I_2 = 1.33 \text{ A}$$

$$I_3 = 1.33 \text{ A}$$

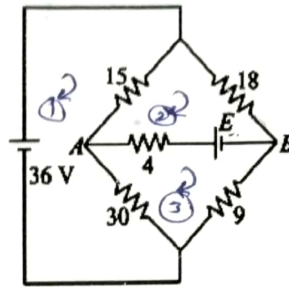


20. Using mesh analysis to find the unknown resistance  $R$  such that the current  $I$  is  $2.88\text{A}$

$$I_1 = 0.48 \text{ A}$$

$$I_2 = 0.28 \text{ A}$$

$$I_3 = -2.6 \text{ A}$$

$$R = 5\Omega$$

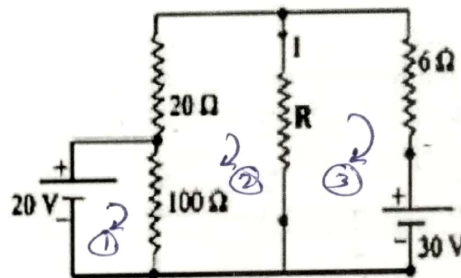


21. Find the voltage  $V_0$  by using mesh analysis

$$V_0 = -21.43 \text{ V}$$

$$I_1 = -3.81 \text{ A}$$

$$I_2 = -4.29 \text{ A}$$

$$I_3 = -10 \text{ A}$$

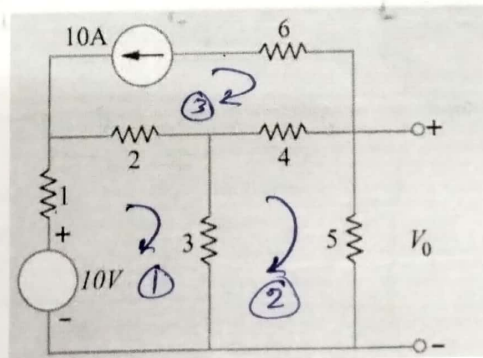


22. Calculate the current  $I_1$ ,  $I_2$  &  $I_3$  by mesh analysis

$$I_1 = -4 \text{ A}$$

$$I_2 = 6.67 \text{ A}$$

$$I_3 = -1.34 \text{ A}$$

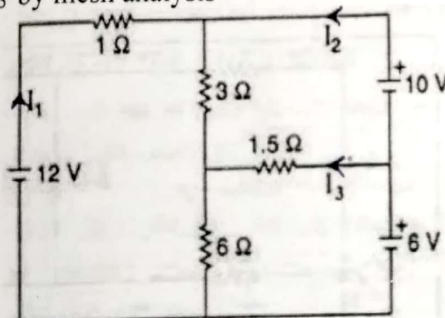




23. Using mesh method, calculate the current through  $2\ \Omega$  resistor.

$$I_1 = 2.69\text{ A}$$

$$I_2 = -0.961\text{ A}$$

$$I_3 = -5\text{ A}$$

$$I_{2\Omega} = 3.651\text{ A}$$

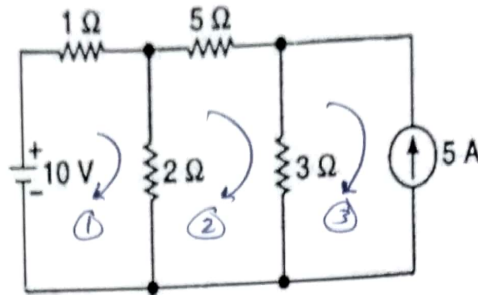

24. Using mesh analysis, find the current through  $6\ \Omega$ ,  $12\ \Omega$  and  $30\ \Omega$  resistor.


$$I_1 = 19.51\text{ A}$$

$$I_2 = 15.37\text{ A}$$

$$I_6 = 9.51\text{ A}$$

$$I_{12} = 5.37\text{ A}$$


$$I_{30} = 4.14\text{ A}$$

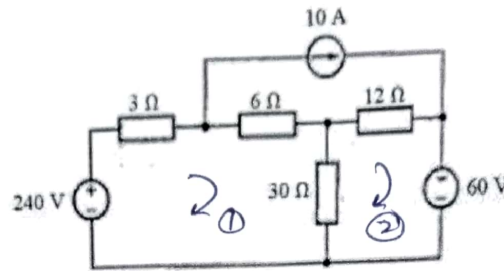

25. Determine the current  $I_x$  through  $10\ \Omega$  resistor (AB branch) and power in  $20\ \Omega$  resistor (CD branch) using mesh analysis.

$$I_x = 1\text{ A (AB)}$$

$$P = 320\text{ W (CD)}$$

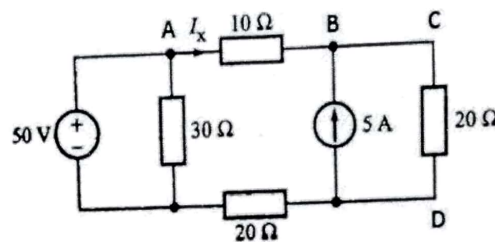


26. Using mesh analysis find  $I_1$ ,  $I_2$  &  $I_3$ .

$$I_1 = 1.91\text{ A}$$

$$I_2 = 3.55\text{ A}$$

$$I_3 = 1.64\text{ A}$$

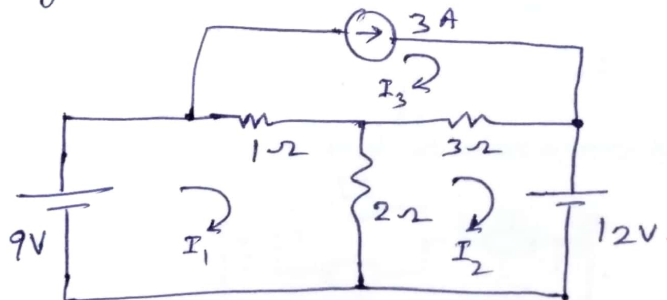


$$I_1 = 4.91\text{ A}$$

$$I_2 = 1.36\text{ A}$$

$$I_3 = 3\text{ A}$$

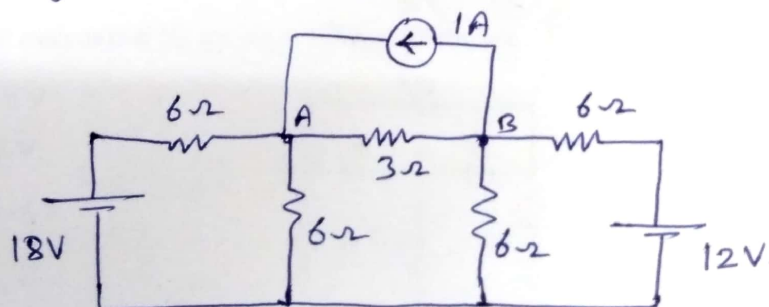27. Using nodal analysis find current in  $3\ \Omega$ .



$$V_A = 9\text{ V}$$

$$V_B = 6\text{ V}$$

$$I = 1\text{ A}$$